 


ECEN 2350: Digital Logic

Assignment #9

1. [5 points.] The file `lab9-q1.v` that you can download from Canvas, contains a testbench for the following circuit, which implements a positive edge-triggered D flip-flop.



Complete `lab9-q1.v` by writing a module that describes the above circuit using gate-level Verilog primitives. Each of the six gates should have a unit delay. Recall that a NAND gate with unit delay, output c , and inputs a, b is written

```
nand #1 (c, a, b);
```

(A primitive gate instance also has an optional instance name, not shown above.) Make sure your simulation results confirm that the circuit you described is a positive edge-triggered D flip-flop. For that, check when the outputs of the circuit change in response to changes in c and d . Submit your completed `lab9-q1.v` file.

2. [2 points.] For the above flip-flop, what is the delay (in simulation time units) from the rising edge of the clock to when the Q -output latches the data? Is it the same if the data is a 0 or 1?

Provide your answer and explanation in a file `lab9-q2.txt`.

3. [8 points.] Make a **shift register** on the Boolean board that works as follows:

The LEDs should display the contents of a 16-bit shift register, that shifts to the right every time push button 0 (e.g. `btn[0]`) is pressed. The shift register should shift in the value of the left-most switch (`sw[15]`).

Note: if you want to use `btn[0]` as a clock (e.g. for use in an `always @(posedge btn[0])` statement), you will need to tell Xilinx to treat the button as a clock input. To do this, add the following code to your constraint (.xdc) file:

```
# Add this to allow btn[0] to be used as a clock
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets btn[0]];
```

If you don't add this, you may get an error stating Poor placement for routing between an IO pin and BUFG that prevents your design from synthesizing. Adding the above to your .xdc file should fix the issue.

A video demonstrating the desired shift-register functionality can be found here:

<https://www.youtube.com/watch?v=ef7ocEqFAoM>

Turn in your Verilog file implementing the shift register as `lab9-q3.txt`.

4. [10 points.] Make a simple 16-bit adding calculator. Your calculator should have two 16-bit operands, *A* and *B*.

When you press `btn[0]`, operand *A* should store the 16-bit number provided on the switches (`sw[15:0]`). When you press `btn[1]`, operand *B* should store the switch value.

At all times, you should display the 16-bit sum $A + B$ in binary on the LEDs.

A video demonstrating the desired functionality can be seen here (enable subtitles to see the A/B register values): <https://youtu.be/kUoNIFW2XNg>

Turn in your Verilog file as `lab9-q4.txt`.